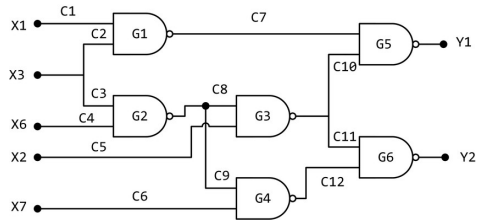



Final project:

Giving circuits as following Fig 1. (a) and (b) show, please answer the following questions:

- (1) Please find the test pattern for these circuits
- (2) Please implement a STUMPS scheme to test the circuits as Fig. 1 (a) and (b) show.



(a)

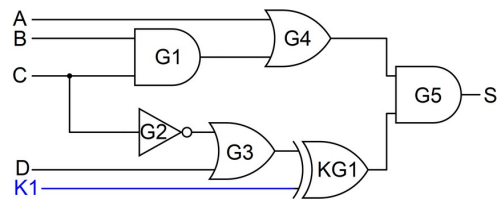

(b)

Fig. 1